

$a$ $x_1 x_2$	$b$ $x_3 x_4$	$f = \text{bigger } (a > b)$
00	00	0
00	01	0
00	10	0
00	11	0
01	00	1
01	01	0
01	10	0
01	11	0
10	00	1
10	01	1
10	10	0
10	11	0
11	00	1
11	01	1
11	10	1
11	11	0

$$f(x_1, x_2, x_3, x_4) = \bar{x}_1 x_2 \bar{x}_3 \bar{x}_4$$

$$\vee x_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 \vee x_1 \bar{x}_2 \bar{x}_3 x_4$$

$$\vee x_1 x_2 \bar{x}_3 \bar{x}_4 \vee x_1 x_2 \bar{x}_3 x_4$$

$$\vee x_1 x_2 x_3 \bar{x}_4$$

$$\Rightarrow f(x_1, x_2, x_3, x_4) = m_4 \vee m_8$$

$$\vee m_9 \vee m_{12} \vee m_{13} \vee m_{14}$$

We now simplify the function using the Karnaugh diagram.

$x_3 x_4$ $x_1 x_2$	00	01	11	10
00				
01	$m_4$			
11	$m_{12}$	$m_{13}$		$m_{14}$
10	$m_8$	$m_9$		

We start the factorization process by forming groups of  $2^k$  minterms.

$$\max_1 = m_{12} \vee m_{13} \vee m_8 \vee m_9 = x_1 \bar{x}_3 \text{ (double fact.)}$$

$$\max_2 = m_{12} \vee m_4 = x_2 \bar{x}_3 \bar{x}_4 \text{ (simple fact.)}$$

$$\max_3 = m_{14} \vee m_{14} = x_1 x_2 \bar{x}_4 \text{ (simple fact.)}$$

We now have the set of maximal monoms:

$$M(f) = \{\max_1, \max_2, \max_3\}$$

The central monoms are the maximal monoms which contain at least one minterm circled once.

We can see that all maximal monoms have such a minterm, so we have the case

$$M(f) = C(f) \Rightarrow \text{1st case of the simplification algorithm}$$

$\Rightarrow$  There is a unique simplified form of  $f$ , obtained as the disjunction of all central monoms:

$$f^s(x_1, x_2, x_3, x_4) = \max_1 \vee \max_2 \vee \max_3$$

$$= x_1 \bar{x}_3 \vee x_2 x_3 \bar{x}_4 \vee x_1 x_2 \bar{x}_4$$

We now can build the simplified logic circuit using only the basic gates AND, OR, NOT.

(Page 4)

Vlad Bogdan-Tudor, 917  
VBD

$$f^s(x_1, x_2, x_3, x_4) = x_1 \bar{x}_3 \vee x_2 x_3 \bar{x}_4 \vee x_1 x_2 \bar{x}_4$$

